

# Lab 3: Cell Characterization using Spectre

Connor Murphy

TA Sina

ECEN454-504

2/25/2022


## Introduction:

In this lab session you will be required to characterize the standard cells that you have used in the design of the pipelined adder so far. Although cell characterization includes a wide number of parameters such as propagation delay, power, area, timing constraints in the case of sequential elements, input capacitance and global parameters like PVT(Process, Voltage, Temperature), corner selection, etc. In this lab you will be dealing only with the propagation delay and input capacitance of a standard cell by performing circuit simulations at the transistor level.

## Results:

### Inverter:

1.

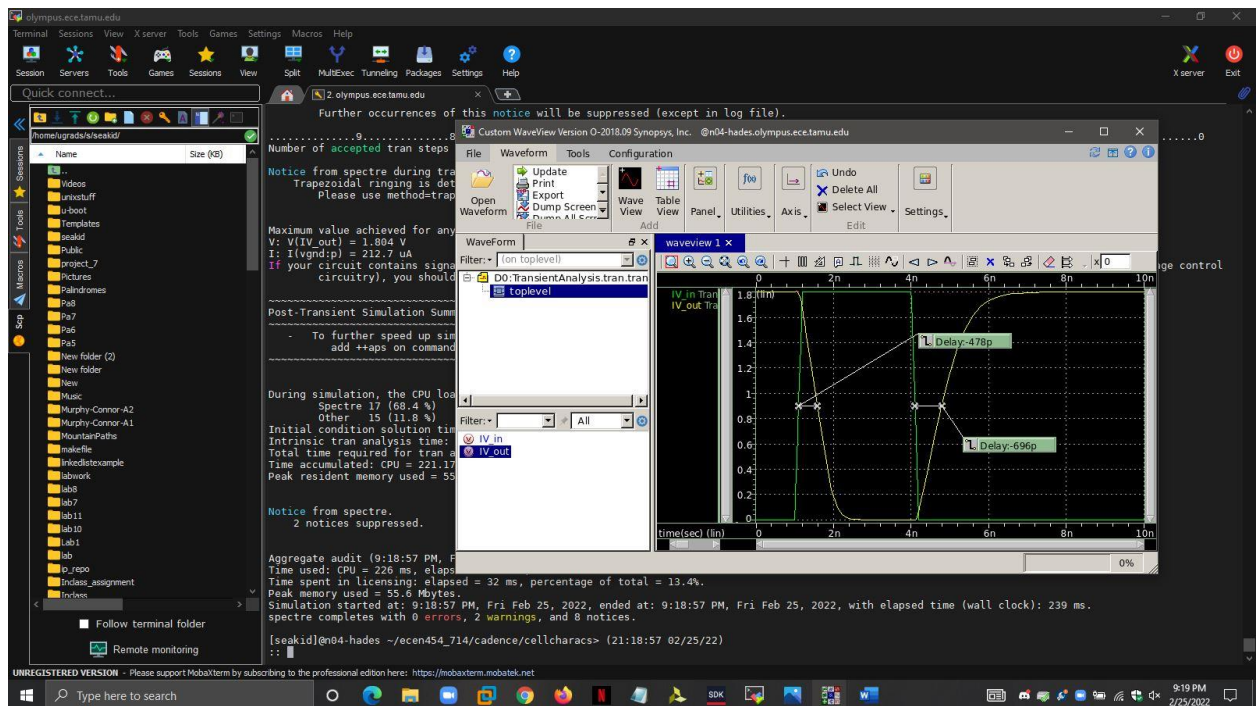

2.

```

inverter - Notepad
File Edit Format View Help
;Spice netlist for an inverter and a capacitor
simulator lang=spectre

include "~/ecen454_714/cadence/cellcharacs/model118.spi"
include "~/ecen454_714/cadence/cellcharacs/cell118.spi"


vgnnd (gnd 0) vsource dc=0
vdd (vdd 0) vsource dc=1.8

vpwl (IV_in 0) vsource type=pwl wave=[0n 0 1n 0 1.2n 1.8 4n 1.8 4.2n 0]

X1 (IV_in IV_out vdd gnd) IV wp=0.6u lp=0.2u wn=0.3u ln=0.2u

R1 (IV_out 1) resistor r=1
C1 (1 0) capacitor c=100f

 TransientAnalysis tran start=0 stop=10ns step=1ps
save IV_in IV_out
  
```




3.

| Capacitance values | Falling Delay | Rising Delay | Error: (Difference of delays/falling delay) |
|--------------------|---------------|--------------|---|
| 100p               | -481p         | -498p        | 3.534%                                      |
| 20p                | -131p         | -144p        | 9.92%                                       |
| 25                 | -153p         | -166p        | 8.49%                                       |
| 30                 | -175p         | -188p        | 7.42%                                       |

|    |       |       |       |
|----|-------|-------|-------|
| 35 | -197p | -210p | 6.59% |
| 40 | -219p | -232p | 5.93% |
| 45 | -240p | -255p | 6.25% |
| 50 | -262p | -276p | 5.34% |
| 55 | -284p | -297p | 4.57% |
| 60 | -306p | -321p | 4.90% |
| 65 | -329p | -325p | 4.86% |
| 70 | -351p | -368p | 4.84% |
| 75 | -373p | -389p | 4.28% |
| 80 | -393p | -410p | 4.32% |


4.

 

Sink capacitance:


| Frequency(MHz) | lfrequency(uA) | Capacitance(ff) |
|----------------|----------------|-----------------|
| 100            | 1.58           | 2.515           |
| 200            | 3.16           | 2.515           |
| 250            | 3.95           | 2.515           |
| 300            | 4.73           | 2.509           |
| 400            | 6.31           | 2.511           |
| 500            | 7.89           | 2.511           |
| 600            | 9.47           | 2.512           |
| 700            | 11.0           | 2.501           |
| 800            | 12.6           | 2.507           |

|                           |      |       |
|---------------------------|------|-------|
| 900                       | 14.2 | 2.511 |
| Sink Capacitance: 2.511fF |      |       |

 


| Capacitance values(fF) | Rising Delay | Falling Delay | Error: (Difference of delays/falling delay) |
|------------------------|--------------|---------------|---|
| 1                      | -38.6p       | -54.9p        | 42.23%                                      |
| 5                      | -74.8p       | -87.2p        | 16.58%                                      |
| 10                     | -109p        | -116p         | 6.42%                                       |
| 20                     | -170p        | -172p         | 1.18%                                       |
| 25                     | -200p        | -200p         | 0.00%                                       |
| 30                     | -232p        | -227p         | 2.20%                                       |
| 40                     | -293p        | -284p         | 3.17%                                       |
| 50                     | -353p        | -341p         | 3.52%                                       |
| 60                     | -416p        | -395p         | 5.32%                                       |
| 70                     | -476p        | -451p         | 5.54%                                       |
| 75                     | -506p        | -478p         | 5.86%                                       |
| 80                     | -535p        | -505p         | 6.14%                                       |
| 85                     | -567p        | -535p         | 5.98%                                       |
| 90                     | -598p        | -562p         | 6.41%                                       |
| 100                    | -658p        | -617p         | 6.65%                                       |

XOR:

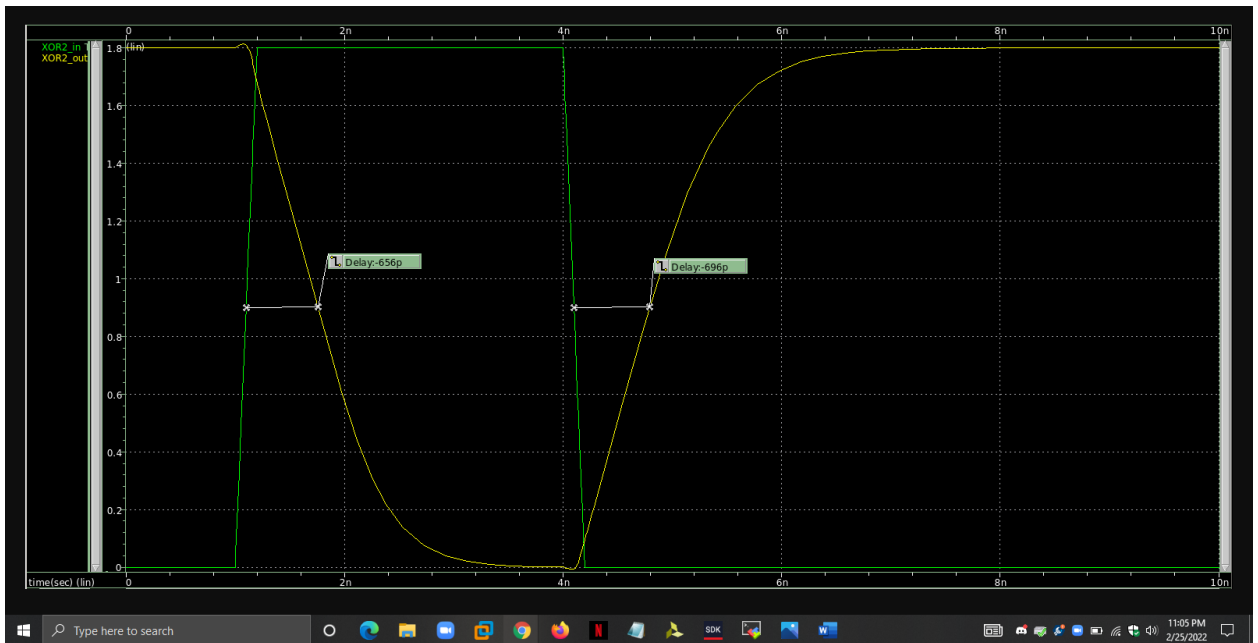

| Capacitance values(fF) | Rising Delay | Falling Delay | Error: (Difference of delays/falling delay) |
|------------------------|--------------|---------------|---|
| 1                      | -41.3p       | -51.3p        | 24.21%                                      |
| 5                      | -70.4p       | -81.7p        | 16.05%                                      |
| 10                     | -103p        | -117p         | 13.59%                                      |
| 20                     | -166p        | -182p         | 9.64%                                       |
| 25                     | -197p        | -214p         | 8.63%                                       |
| 30                     | -228p        | -247p         | 8.33%                                       |
| 40                     | -290p        | -311p         | 7.24%                                       |
| 50                     | -351p        | -374p         | 6.55%                                       |
| 60                     | -412p        | -441p         | 7.40%                                       |
| 70                     | -473p        | -503p         | 6.34%                                       |
| 75                     | -504p        | -537p         | 6.55%                                       |
| 80                     | -535p        | -569p         | 6.36%                                       |
| 85                     | -566p        | -599p         | 5.83%                                       |
| 90                     | -596p        | -633p         | 6.21%                                       |
| 100                    | -656p        | -696p         | 6.10%                                       |

 

| Frequency(MHz)            | Ifrequency(uA) | Capacitance(fF) |
|---------------------------|----------------|-----------------|
| 100                       | 4.89           | 7.783           |
| 200                       | 9.77           | 7.775           |
| 250                       | 12.2           | 7.767           |
| 300                       | 14.7           | 7.799           |
| 400                       | 19.5           | 7.759           |
| 500                       | 24.4           | 7.653           |
| 600                       | 29.3           | 7.764           |
| 700                       | 34.2           | 7.771           |
| 800                       | 39.0           | 7.7789          |
| 900                       | 43.9           | 7.775           |
| Sink Capacitance: 7.772fF |                |                 |

5.

```
cell18 - Notepad
File Edit Format View Help
//Spice netlist for an inverter
simulator lang=spectre
subckt IV (input output VDD VSS)
    parameters wp=0.6u lp=0.2u wn=0.3u ln=0.3u
    M1 output input VDD VDD tsmc18P w=wp l=lp
    M2 output input VSS VSS tsmc18N w=wn l=ln
ends IV

subckt NAND2 (A B output VDD VSS)
    parameters wp=0.6u lp=0.2u wn=0.3u ln=0.2u
    //PMOS
    M1 output A VDD VDD tsmc18P w=wp l=lp
    M2 output B VDD VDD tsmc18P w=wp l=lp
    //NMOS
    M3 output A wire1 VSS tsmc18N w=wn l=ln
    M4 wire1 B VSS VSS tsmc18N w=wn l=ln
ends NAND2

subckt XOR2 (A B output VDD VSS)
    parameters wp=0.6u lp=0.2u wn=0.3u ln=0.3u
    //PMOS
    M1 wire1 B VDD VDD tsmc18P w=wp l=lp
    M2 output inv_A wire1 VDD tsmc18P w=wp l=lp
    M3 wire2 inv_B VDD VDD tsmc18P w=wp l=lp
    M4 output A wire2 VDD tsmc18P w=wp l=lp
    //NMOS
    M5 output inv_A wire3 VSS tsmc18N w=wn l=ln
    M6 wire3 inv_B VSS VSS tsmc18N w=wn l=ln
    M7 output A wire4 VSS tsmc18N w=wn l=ln
    M8 wire4 B VSS VSS tsmc18N w=wn l=ln
    //Inverter_A
    M9 inv_A A VDD VDD tsmc18P w=wp l=lp
    M10 inv_A A VSS VSS tsmc18N w=wn l=ln
    //Inverter_B
    M11 inv_B B VDD VDD tsmc18P w=wp l=lp
    M12 inv_B B VSS VSS tsmc18N w=wn l=ln
ends XOR2
```

Ln 37, Col 10 100% Unix (LF) UTF-8 10:37 PM 2/25/2022