

Lab 6: Design and Characterization of a Flip-Flop

Connor Murphy

TA Sina


ECEN-454-507

3/26/2022

Introduction:

After completing the design of a single combinational stage of the design, you will next design the basic sequential element that will be used in the design, i.e., the Flip-Flop (FF). In this lab you will be required to design Flip-Flop and also characterize its delay, input capacitance and its setup and hold time.

Results:

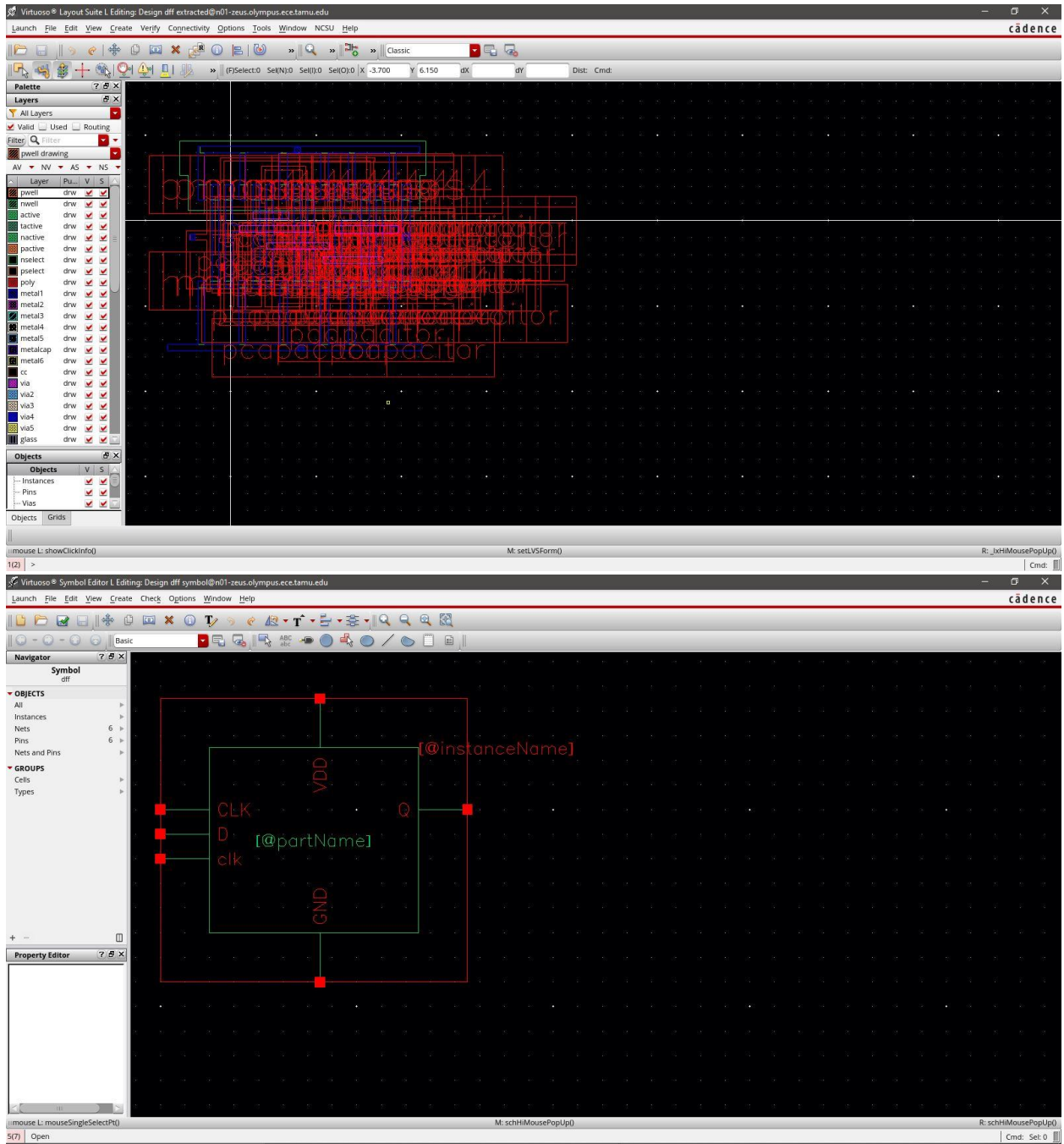

Devices in the netlist but not in the rules:
pcapacitor pmos nmos

The net-lists match.

	layout	schematic
instances		
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	20	20
total	20	20
nets		
un-matched	0	0
merged	0	0
pruned	0	0
active	13	13
total	13	13
terminals		
un-matched	0	0
matched but		
different type	2	2
total	6	6

Probe files from /home/ugrads/s/seakid/cadence/LVS/schematic

devbad.out:

netbad.out:


mergenet.out:


termbad.out:

? Terminal CLK's type in the schematic: inputOutput, in the layout: input
? Terminal _CLK's type in the schematic: inputOutput, in the layout: input


prunenet.out:

prunedev.out:

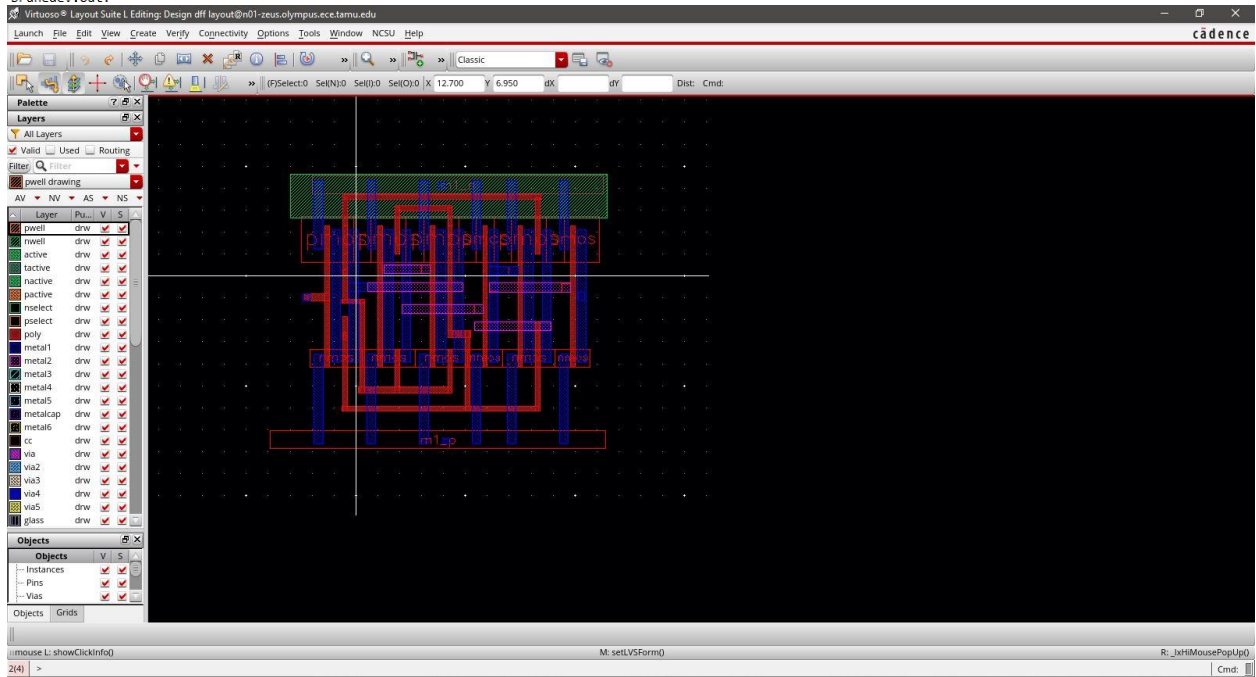

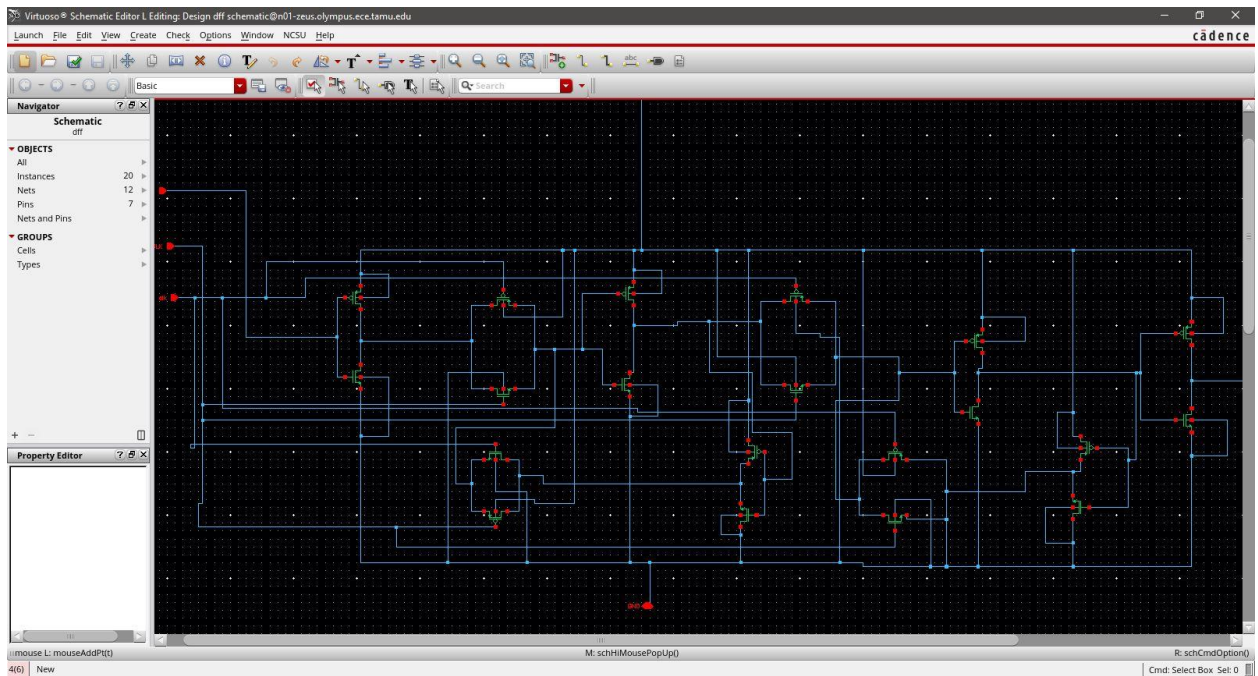

Transient Response

 

Transient Response

Name

/CLK


/CLK

/D

/Q

/V3/MINUS

/V3/PLUS

 

AC Response

Name

■ /V4/MINUS

